

1a)

$$\left| \frac{0.814215 - 9_{11}}{9_{11}} \right| \times 100\% = 0.485$$

1b)

$$\left| \frac{0.91871 - 9_{11}}{9_{11}} \right| \times 100\% =$$

LAB REPORT (Weight: 50%)


PART (A) : ERROR ANALYSIS: Calculate the error observed in the experimentally determined $R_{in}(Expt)$ and in the ohmmeter-measured value $R_{in}(OM)$ with respect to the theoretical value $R_{in}(calc)$. Comment on the results.

1) Error in $R_{in}(expt) = 100 [R_{in}(expt) - R_{in}(calc)] / R_{in}(calc) = \dots 0.485 \dots \%$

2) Error in $R_{in}(OM) = 100 [R_{in}(OM) - R_{in}(calc)] / R_{in}(calc) = \dots 0.0646 \dots \%$

PART (B) : TEC & MPT :

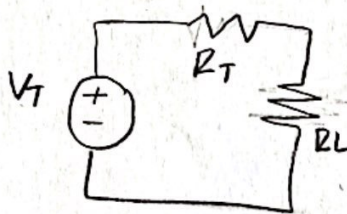- (a) Calculate the value of V_T and R_T from the data of Steps 7 & 8
Draw the TEC in the space provided below.



$$V_T \text{ from 7} = 11.5684 \text{ V}$$

$$R_L = 1180 \Omega$$

$$V = RI$$

$$\frac{V}{R} = I$$


For P_{max} we know $R_L = R_T$

$$P_{max} = VI \Rightarrow V \cdot \frac{V}{R}$$

$$\frac{V^2}{R} = \frac{11.5684^2}{4(1180)}$$

- (b) The maximum power available from the TEC is $P_{max} = \dots 0.02835 \dots \text{W}$

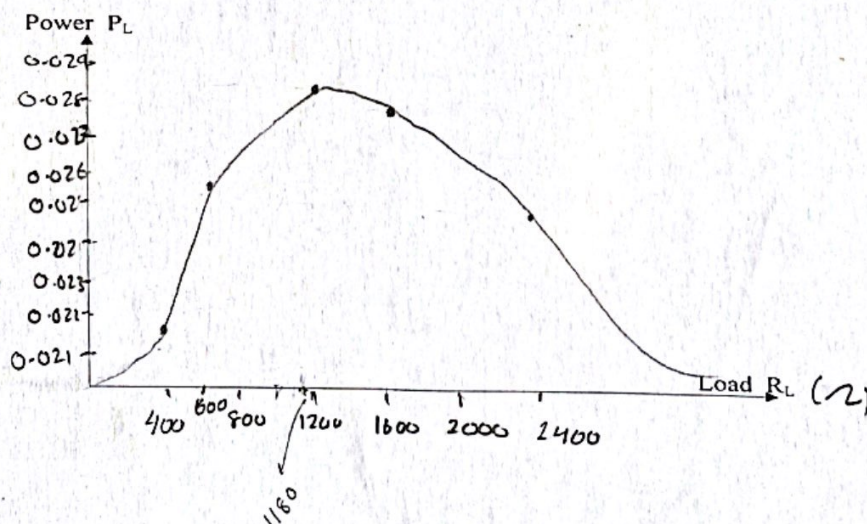- (c) Plot P_L against the five selected values of R_L in the co-ordinate space provided below :



MANU EISNER 4/21/24

(LAB RECORD Continued)

Maximum Power Transfer Theorem Verification : [Step 9]

Nominal Load Resistor (R_L) Values used: [Note: $R_a < R_b < R_T$ and $R_d > R_c > R_T$]

[$R_L = R_T$ when $V_L = V_T/2$]

$R_a = \dots 400 \dots \Omega$, $R_b = \dots 600 \dots \Omega$,

$R_c = \dots 1600 \dots \Omega$, $R_d = \dots 2400 \dots \Omega$,

Load Resistance $R_L \Omega$	Load Voltage V_L volts	$P_L = (V_L)^2/R_L$ (W) or mW
$R_a = 400$	2.9408	0.02162
$R_b = 600$	3.9099	0.025479
R_L^{1180} (for $V_T/2$)	5.7843	0.028354
$R_c = 1600$	6.6563	0.027691
$R_d = 2400$	7.7519	0.025038

TA signature : MP